

Communications & Computer science Shoubra faculty of engineering Benha university

Power supply

Ву


Group 7

Supervised by


Dr. Emad

2023-2024

Schematic:

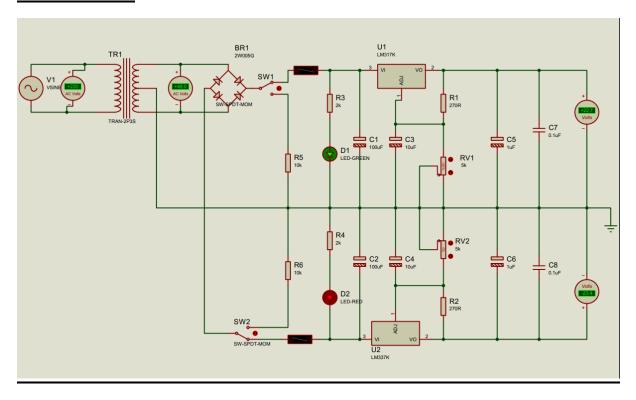


Project Mechanism:

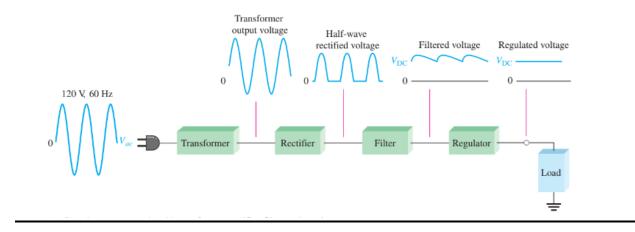


Data Sheet:


Symbol	Value	
TR1	220V to 24/-24	
BR1	Bridge	
SW1, SW2	Switch	
R1, R2	270 ohm	
R3, R4	2k-ohm	
R5, R6	10k-ohm	
D1, D2	Diode	
C1, C2	100 uF	
C3, C4	10 uF	
C5, C6	1 uF	
C7, C8	0.1 uF	
U1	LM317K	
U2	LM337K	
RV1, RV2	5k-ohm	

Layout:

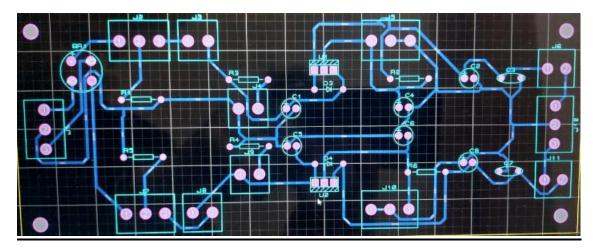


<u>3D:</u>

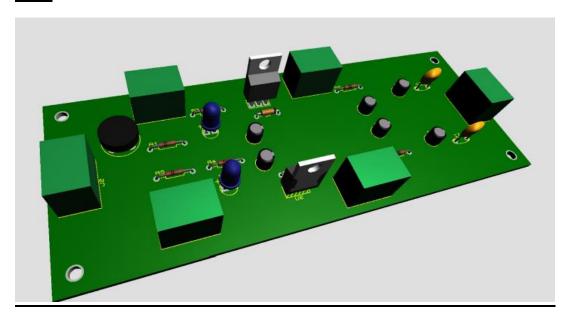

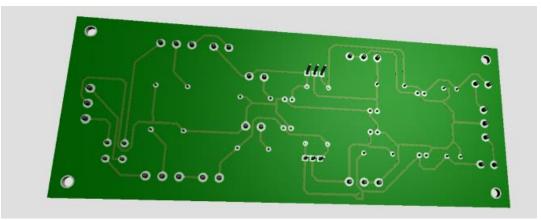


Test:



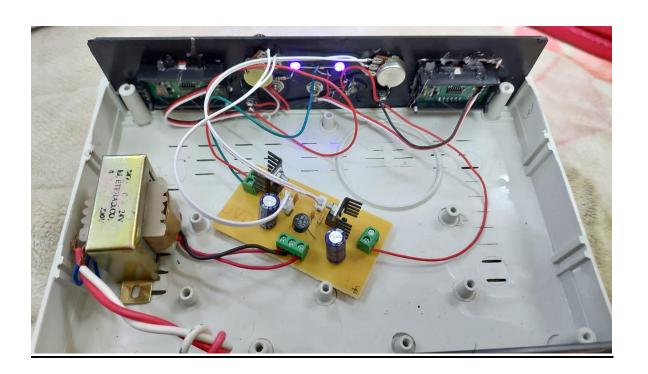

Tracks:

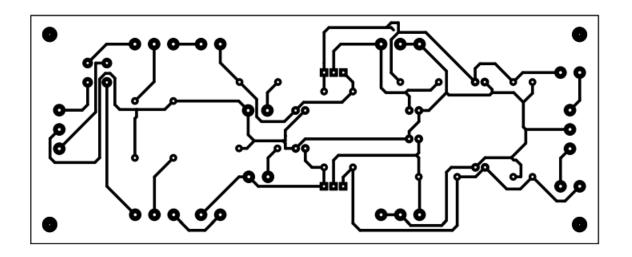

This project made by:

الاسم	رقم التسلسل
زياد بلال جمال الدين الصياد	26
زياد محمد عبدالفتاح فهيم	27
على محمد على شريف	37
كريم إيهاب محمد عطيه	40
كيرلس هاني سلامه عبدة	41